ELEC 402

Standard Cell Layout Lecture 10


Reza Molavi
Dept. of ECE
University of British Columbia
reza@ece.ubc.ca

Slides Courtesy: Dr. Sudip Shekhar (UBC)




Gate Layout

- Layout can be very time consuming
 - Design gates to fit together nicely
 - Build a library of standard cells
 - Use PNR (placement & routing) tools for synthesis
- Standard cell design methodology
 - V_{DD} and GND should abut (standard height)
 - Adjacent gates should satisfy design rules so as to "snap together"
 - NMOS at bottom and PMOS at top
 - All gates include well and substrate contacts
 - Use poly and M1 to route the standard cells v_o and leave upper metal layers (M2, M3...) as routing channels to interconnect cells
 - Upper metal layers often follow HVH or VHV track direction to ease PNR

 




Standard Cells – Inverter

 


- Horizontal N-diffusion and P-diffusion strips, Vertical polysilicon gates
- ➤ Metal1 V_{DD} and GND rails at top and bottom respectively
- $\lambda = 0.125 \, \mu \text{m}$ in 0.25 μm process \rightarrow not that useful in newer technologies



Standard Cells - NAND2

 

2-input NAND gate

 

Standard Cell Layout Methodology


Mirrored Cell V_{DD} V_{DD} M2 M3 **GND** Mirrored Cell **GND**

Contacts & Wells not shown



Pitch Matching of Snap-Together Cells

 The two technique allowing to repeat structures and abut them together






Pitch matching is a necessity



Pitch Matching of Snap-Together Cells

 The two technique allowing to repeat structures and abut them together






Pitch matching is a necessity




Multi-Fingered Transistors

 


For a very wide transistor that does not fit in the standard cell height, break the transistor into multiple fingers → wide layout

Stick Diagrams

- Contains no dimensions
- Represents relative positions of transistors
- > Help plan layout quickly

 

 

NAND3

Stick Diagrams Example: **O3AI**


The goal is to draw the layout such that

- there is <u>no</u>
 <u>discontinuity</u> in
 diffusion areas
- 2. gates (polysilicon in red) run vertically
- 3. No need for <u>crossovers</u>

M1 (first metal layer) is drawn in blue to make necessary connections




Stick Diagrams & Logic Graph

 

- Systematic approach to derive order of input signal wires so gate can be laid out to minimize area
- ➤ PU and PD are duals (parallel ←→ series)
- Vertices are nodes (signals) of circuit, VDD, X, GND; Edges are transistors




Two Possibilities

 

- > Line of diffusion layout abutting source-drain connections
- Crossover eliminated by A B C ordering


Consistent Euler Trail

 
- > ABC
- > CAB
- \triangleright B C A \rightarrow no PD
- > BAC
- \triangleright ACB \rightarrow no PD
- > CBA




- > A path through all nodes in the graph such that each edge is visited once and only once.
- > The sequence of signals on the path is the signal ordering for the inputs.
- > PU and PD Euler paths are (must be) consistent (same sequence)
- > If you can define a Euler path then you can generate a layout with no diffusion breaks


Example 2: AOI22 x = (ab+cd)'

 

 

 


(b) Euler Paths $\{a \ b \ c \ d\}$

 


(c) stick diagram for ordering $\{a\ b\ c\ d\}$


Circuit Diagram


Example 3: Y = (ab+c+d)'

 


 

NAND3 with Good Layout

 

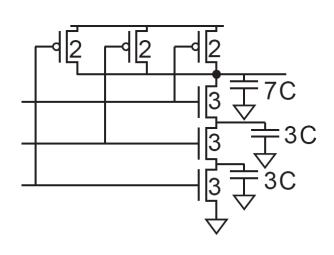

 

Actual diffusion cap on the output is 7C, instead of 9C

Example 4 and Key Solution

Out' = a(d+e) + bc

