

---

# ELEC 402


## Dynamic Logic Design (Transfer Gates) Lecture 11

Reza Molavi  
Dept. of ECE  
University of British Columbia  
reza@ece.ubc.ca

Slides Courtesy : Dr. Res Saleh (UBC), Dr. D. Sengupta (AMD), Dr. B. Razavi (UCLA)

---


# Static vs. Dynamic Logic Design

 

PMOS typically  
2-times NMOS  
For symmetric  $T_{PHL}/T_{PLH}$
 
## CMOS Logic

- No static power consumption
- Ideal  $V_{OL}$  and  $V_{OH}$
- Symmetric rise and fall achievable
- Complementary pull-up required (area)



NMOS typically  
4-times NMOS  
For symmetric low  $V_{OL}$


## Pseudo-NMOS Logic

- Single pull-up device only
- Degraded  $V_{OL}$  (ratioed inverter)
- Static power when output is low
- Asymmetric rise/fall times


A solution which is both Fast and Area-efficient

# Pass Transistor – Dynamic Storage Concept


## NMOS

 


(a)

 


(c)

 


## PMOS

 

(b)

 

(d)

 

Good


A bit problematic

Transfers an input signal unaltered to the output when gate is **ON**

Hold the output value on output Capacitance when the gate is **OFF** (High – Z)

- Not always a DC path to Gnd or supply
- Prone to error from environment

# Single Pass Transistor Shortcoming

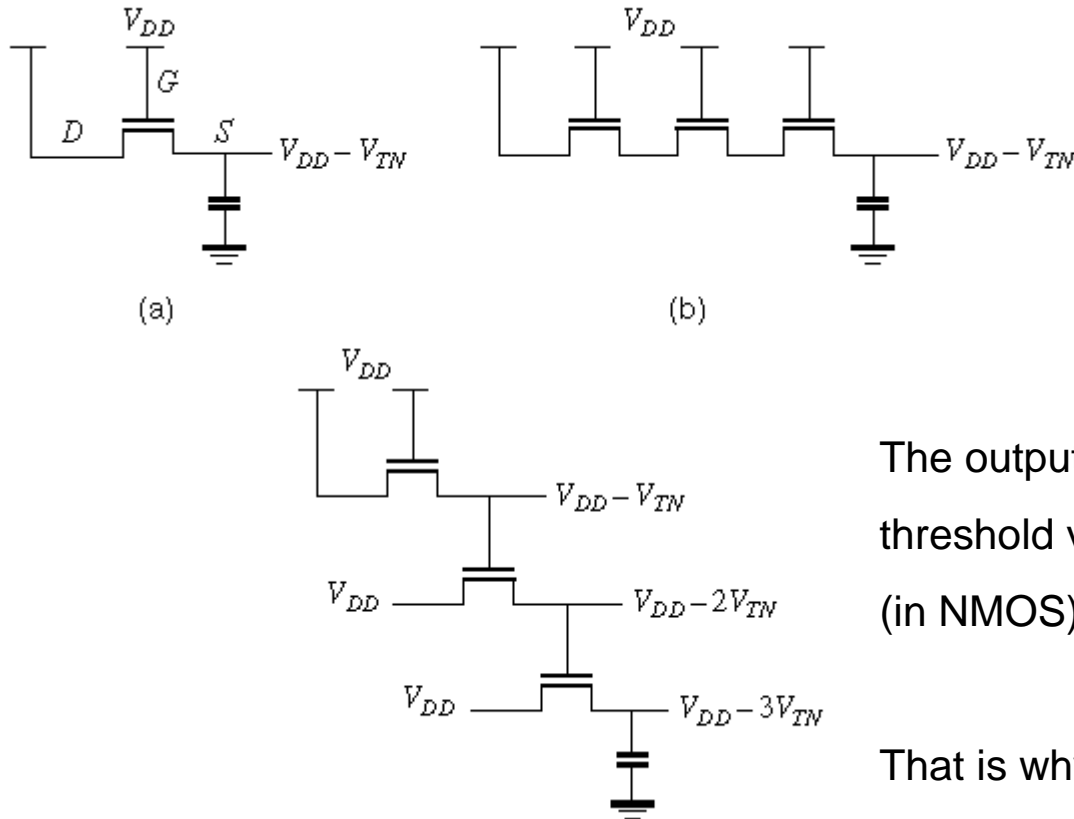



The output can only climb up within one threshold voltage ( $V_t$ ) of voltage applied to gate (in NMOS) – opposite applies for PMOS

That is why (a) and (b) produce the same output but (c) is a different output voltage. .

# Issues with Pass Transistors
  
## Capacitive feed through

- Just as the switch (pass gate) is turning off there might be sudden change in the output value due to capacitive voltage division between the  $C_f$  and output capacitance ( $C_{gnd}$  in the figure)
- Not desirable, the stored value would be different/degraded




(a) Positive feedthrough

(b) Negative feedthrough

Case (a) is an issue for PMOS

Case (b) is an issue for NMOS

# Capacitive Feedthrough

 


(a) Positive feedthrough

(b) Negative feedthrough

Charge equilibrium between two  
Series-connected capacitors

$$C_f(V_1 - V_2) = C_{\text{gnd}}V_2$$
 
$$V_2 = \frac{C_f V_1}{C_f + C_{\text{gnd}}}$$




If abrupt  
change in  $V_1$

$$\Delta V_2 = \frac{C_f \Delta V_1}{C_f + C_{\text{gnd}}}$$

We need to know the value of  $C_{\text{GS}}$  and  $C_{\text{out}}$  to  
Properly calculate this change (need to know what  
**Region of operation** the switch is **throughout the change**)

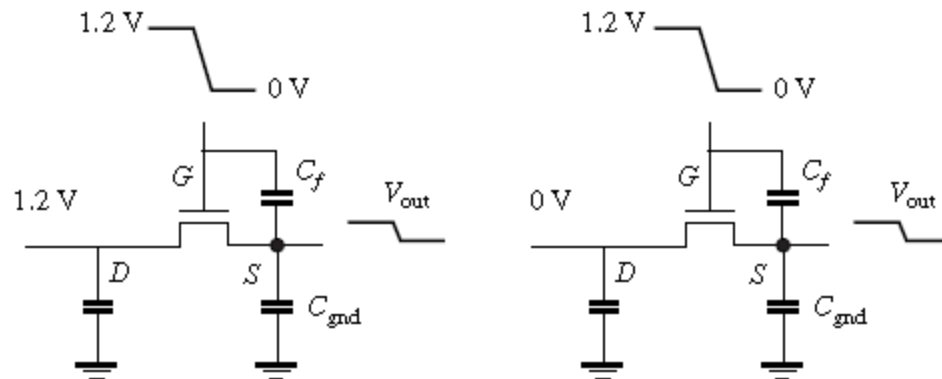
# Capacitive Feedthrough - Example

In the circuit below with the input at 1.2 V, what is the initial value of the output when the clock is at 1.2 V. Estimate the final value after the clock goes low. Repeat the problem for the case when the input is 0 V. Assume that the device is  $4\lambda/2\lambda$  in  $0.13\ \mu\text{m}$  technology.


 
# Charge Sharing

If two isolated nodes with different voltages are suddenly Connected they would share the charge,  
may degrade the stored value



$$Q_{\text{total}} = C_1 V_1 + C_2 V_2$$

before

$$Q_{\text{total}} = (C_1 + C_2) V^*$$

after

$$V^* = \frac{(C_1 V_1 + C_2 V_2)}{C_1 + C_2}$$

New voltage

- Note that after charge sharing (switch turning on) there should still be  $V_T$  drop across  $V_{GS}$
- Otherwise the source would not exceed  $V_{DD} - V_T$  (see next example)




# Charge Sharing – Example

In Figure 7.6a, compute the charge-sharing effects for the following cases assuming 0.13  $\mu\text{m}$  technology parameters:

(a)  $C_1 = 100 \text{ fF}$ ,  $C_2 = 20 \text{ fF}$ ,  $V_1 = 0$ ,  $V_2 = 1.2 \text{ V}$

(b)  $C_1 = 20 \text{ fF}$ ,  $C_2 = 20 \text{ fF}$ ,  $V_1 = 0$ ,  $V_2 = 1.2 \text{ V}$

 (c)  $C_1 = 20 \text{ fF}$ ,  $C_2 = 100 \text{ fF}$ ,  $V_1 = 0$ ,  $V_2 = 1.2 \text{ V}$



(Board Notes)


$$(a) V^* = \frac{(C_1 V_1 + C_2 V_2)}{C_1 + C_2} = \frac{(100 \text{ fF} \times 0 + 20 \text{ fF} \times 1.2)}{(20 \text{ fF} + 100 \text{ fF})} = 0.2 \text{ V}$$

$$(b) V^* = \frac{(C_1 V_1 + C_2 V_2)}{C_1 + C_2} = \frac{(20 \text{ fF} \times 0 + 20 \text{ fF} \times 1.2)}{(20 \text{ fF} + 20 \text{ fF})} = 0.6 \text{ V}$$


$$(c) V^* = \frac{(C_1 V_1 + C_2 V_2)}{C_1 + C_2} = \frac{(20 \text{ fF} \times 0 + 100 \text{ fF} \times 1.2)}{(20 \text{ fF} + 100 \text{ fF})} = 1.0 \text{ V} \rightarrow$$

That is more than  $V_{DD} - V_T$ , therefore  
One side clips to  $V_{DD} - V_T$  and the rest  
of charge determines the voltage at  
other node

# CMOS Transmission Gate

 

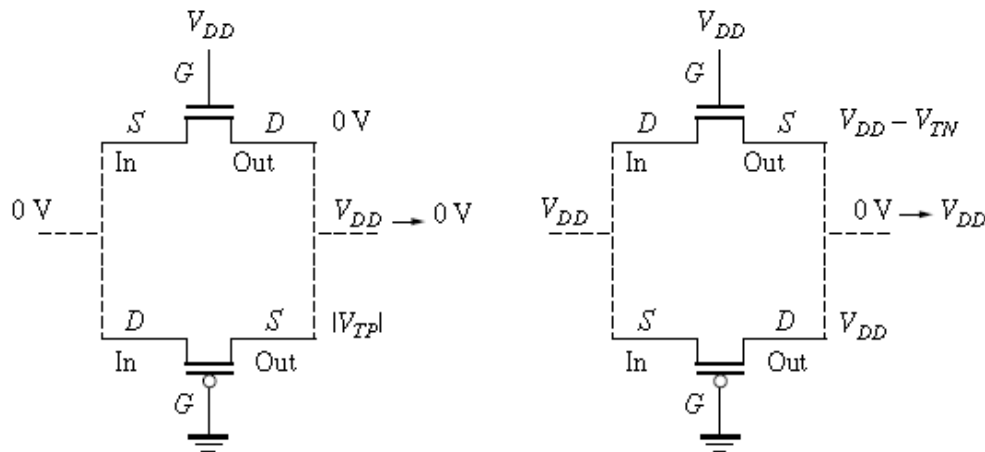Using both control (C) signal and its complementary ( $\bar{C}$ ) to pass the signal



(Board Notes)


How about clock

Feedthrough?


Is it better or worse than single

The combination of both devices allows proper passage of signal (always one **Strong** and one **Weak** device)


# Logic Circuit Design Using TGs

 

XOR

 



XNOR

 

MUX2

- When two TGs are shorted at output, it does '+' operation (like OR)
- When a TG passes 'A' signal with 'C' control, it does '.' operation (like AND)


## Example – MUX4 implementation

  

Which one is faster? We need to quantify the speed just like what we did with CMOS


Logic gates

# Important Design Note

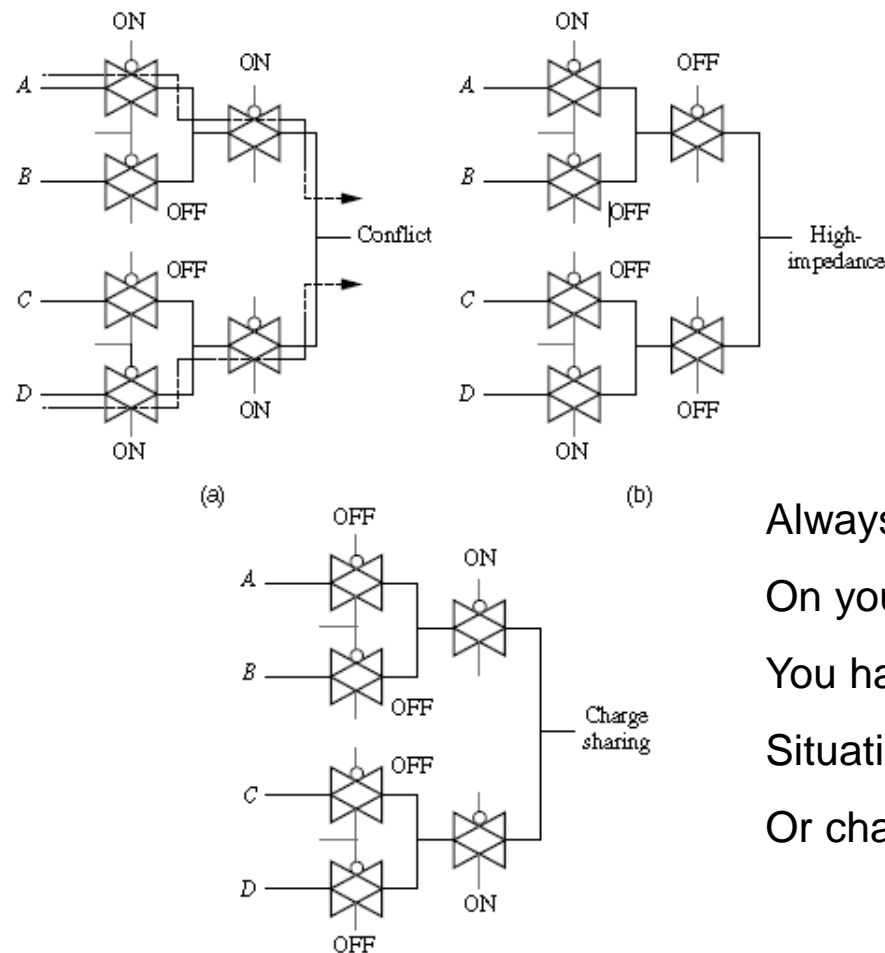

Always do a sanity check  
On your TG design to ensure  
You have avoided all problematic  
Situations (multiple path, no path  
Or charge sharing scenario)

# Custom Logic Design Using TGs

 


(Board notes)

Q: Is NMOS of TG needed in OR circuit?

- Strategy:
1. Pick a few of your variables as control signal
  2. Build a truth table
  3. Implement using simple AND/OR/MUX structures introduced
  4. Simplify the circuit (if possible)

**Example:** Implement the function  $F = AB + \overline{A}\overline{B}C + \overline{A}\overline{B}\overline{C}$  using transmission gates.

# TG Delay Calculation

 


We need to calculate  $R_N$  and  $R_P$  and their equivalent parallel resistance

Let's start with the case that we are propagating 0 (A is 0 and B is at  $V_{DD}$  but transitioning To 0),

NMOS is partly in Saturation, partly in linear region  $R_N = \frac{V_{out}}{I_{Dsat,n}}$   $R_N = \frac{V_{out}}{I_{Dlin,n}}$

PMOS is in saturation till output reaches  $V_T$  and then is off)  $R_P = \frac{V_{out}}{I_{Dsat,p}}$

# TG Delay Calculation - II

 


(a)  $V_{in} = 0 \text{ V}$ ,  $V_{out} = V_{DD} \rightarrow 0 \text{ V}$


- NMOS resistance decreases as device enters linear from saturation (remember  $I_{deminas}$  vs  $V_{ds}$  curve)
- PMOS resistance goes to infinity at  $V_T$  (switch turns-off)
- The average of value of PMOS resistance roughly is twice that of its saturation value,  $R_P \sim 2R_{eqp}$
- The parallel combination of the two resistances remains constant!



# TG Delay Calculation - Resistance

 

 (a)  $V_{in} = 0\text{ V}$ ,  $V_{out} = V_{DD} \rightarrow 0\text{ V}$



(b)  $V_{in} = V_{DD}$ ,  $V_{out} = 0\text{ V} \rightarrow V_{DD}$

$$R_{TG} = R_N // R_P = R_{eqn} // 2R_{eqp} \approx R_{eqn} // 4.8R_{eqn} = 0.83R_{eqn} \approx R_{eqn}$$

$$R_{TG} = R_N // R_P = 2R_{eqn} // R_{eqp} \approx 2R_{eqn} // 2.4R_{eqn} = 1.1R_{eqn} \approx R_{eqn}$$


Similar Unit resistance due to parallel combination of structures

PMOS and NMOS can be chosen equal size in TG

$$R_{TG} = R_{eqn} \left( \frac{L}{W} \right)$$

Scale with proper W/L

# TG Delay Calculation - Capacitance

 


(a) OFF state

$$C_{in} = C_{out} = C_{eff}(W_n + W_p)$$

$$C_{in} = C_{out} = C_{eff}2W$$

 Devices are off, no contribution from gate  
Capacitance, Equal devices



(b) ON state

$$C_{in} = C_{out} = C_{eff}(W_n + W_p) + \frac{1}{2}(C_g W_n + C_g W_p)$$


$$C_{in} = C_{out} = C_{eff}2W + C_g W$$

Devices are in linear, half the gate capacitance to  
Source & drain, Equal devices
 
# Elmore Delay - Review

---

Useful technique to find a quick hand calculation for RC delay for long chains



$$\tau = R_1 C_1 + (R_1 + R_2) C_2 + (R_1 + R_2 + R_3) C_3$$

$$\tau_i = \sum_k (C_k \times R_{ik})$$


Where  $\Gamma_i$  is the total delay, you have to sum all the RC components in the following steps:

1. Highlight the main path, sum all R's and multiply up by the final  $C_{\text{main}}$
2. Find the common resistors between the main path and any other path ( $R_X$ ) that contains a  $C_X$
3. Sum all the components  $\Gamma_i = \sum R_X C_X + R_{\text{main}} C_{\text{main}}$
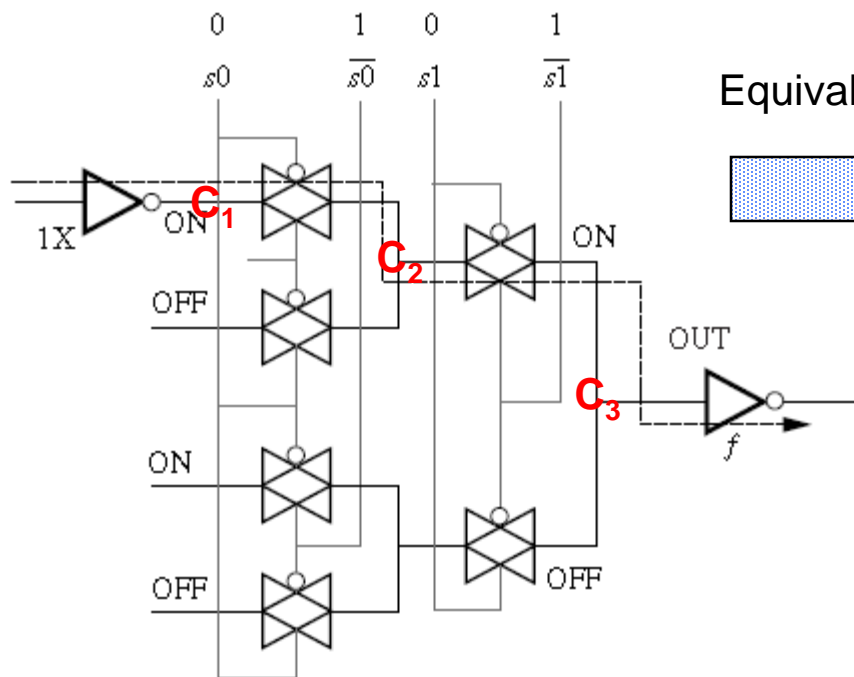
# TG Delay Calculation – Cont'd



Now using Elmore delay and TG delay calculations we can answer last the question

Which of the two MUX4 implementations (slide 12) are faster(assume fan-out of f times 1x inverter)?



**Implementation I**

Equivalent model

  

$$t_1 = R_{inv}C_1 + (R_{inv} + R_{TG})C_2 + (R_{inv} + 2R_{TG})C_3 \quad \text{From Elmore}$$

$$C_1 = 3C_{eff}W + C_gW + 2C_{eff}W$$


$$C_2 = C_gW \times 2 + 2C_{eff}W \times 3$$

$$C_3 = 2C_{eff}W \times 2 + C_gW + 3fC_gW$$

$$t_1 = R(29C_{eff} + 8C_g + 9fC_g)W$$



$$R_{inv} = R_{TG} = R$$

# TG Delay Calculation – Cont'd

 

**Implementation II**

Equivalent model

  

$$t_2 = R_{inv}C_4 + (R_{inv} + R_{TG})C_5 \quad \text{From Elmore}$$

$$C_4 = 3C_{eff}W + 2C_{eff}W + C_gW$$

$$C_5 = 2C_{eff}W \times 4 + C_gW + 3fC_gW$$

$$t_2 = R(21C_{eff} + 3C_g + 6fC_g)W$$

$$R_{inv} = R_{TG} = R$$

**Faster**

Note that the loading of ON and OFF transmission gates are different!