 

ELEC 403

Delay & Static CMOS Logic Lecture 8 & 9

Reza Molavi
Dept. of ECE
University of British Columbia
reza@ece.ubc.ca

Slides Courtesy : Dr. Res Saleh (UBC), Dr. Sudip Shekhar (UBC), Dr. B. Razavi (UCLA)

Different Delay Definitions



“Delay” $\rightarrow t_{pd}$

Max-time \rightarrow Propagation time

Min-time \rightarrow Contamination time

Rise Time (t_r , t_{LH}): time taken to rise from 10% to 90% (sometimes 20% to 80%) **Fall Time (t_f , t_{HL}):** time taken to drop from 90% to 10% (sometimes 80% to 20%) **Edge Rate (t_{rf}):** $(t_r + t_f)/2$.

Rise propagation delay (t_{pdr} , t_{pLH}): maximum time from the input crossing 50% to output crossing 50%, with output rising





Fall propagation delay (t_{pdf} , t_{pHL}): maximum time from the input crossing 50% to output crossing 50%, with output falling

Propagation Delay (t_{pd}): $(t_{pHL} + t_{pLH})/2$.

Contamination Delay (t_{cd}): minimum time from the input crossing 50% to the output crossing 50%.

Inverter – Sizing

    - In ratioed logic families (such as diode-connected load or pseudo NMOS, V_{OL} is a priority so the Size of load is mainly determined by the choice of V_{OL}
- In non-ratioed logic families (such CMOS inverters) propagation delay is important



Pull-down (output capacitor discharge)
through the NMOS transistor



$$V_{out}(t) = V_{DD} e^{-t/R_N C_L}$$

T_{PHL} is the time it take for the capacitor to
discharge to 50% of the final value

(Board notes)

Effective Resistance Calculations

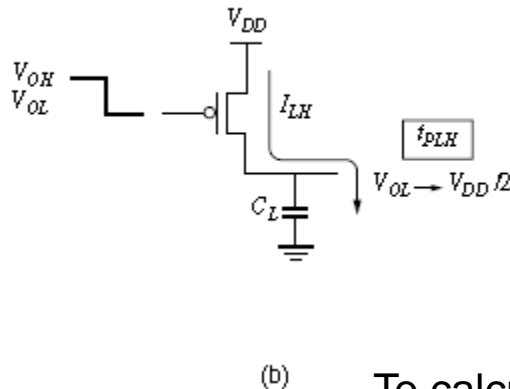 
Calculate the delay from the charge/discharge of capacitor



$$I = C_L \frac{dV}{dt} \rightarrow \Delta t \approx \frac{C_L \Delta V}{I_{DS}}$$

$$t_{PHL} = \frac{C_L (V_{DD}/2)}{I_{HL}}$$

To calculate I_{HL}

 

$$V_{DD} = 1.2 \text{ V}, V_T = 0.4 \text{ V}, \text{ and } E_{CL} = 0.6 \text{ V}$$

$$V_{Dsat} = \frac{(V_{GS} - V_T) E_{CL}}{(V_{GS} - V_T) + E_{CL}} = \frac{(1.2 - 0.4)(0.6)}{(1.2 - 0.4) + (0.6)} \cong 0.34 \text{ V}$$

NMOS remains in Saturation throughout T_{PHL}

$$t_{PHL} = \frac{C_L (V_{DD}/2)}{(I_{Dsat})_n}$$

$$R_N = \frac{V_{DD}/2}{0.7 (I_{Dsat})_n}$$

Effective Resistance Calculations

Problem:

Using 0.13 μm technology parameters, compute R_{eqn} and R_{eqp} from the equations above for unit-sized devices.

Solution:

For the NMOS device,

$$\begin{aligned} I_{Dsat} &= \frac{W_N \mu_{sat} C_{ox} (V_{DD} - V_{TN})^2}{(V_{DD} - V_{TN}) + E_{CN} L_N} \\ &= \frac{(0.1)(10^{-4})8(10^6)1.6(10^{-6})(1.2 - 0.4)^2}{(1.2 - 0.4) + 0.6} \approx 60 \mu\text{A} \end{aligned}$$

$$\therefore R_{eqn} = \frac{1.2/2}{0.7(60 \mu\text{A})} = 14.5 \text{ k}\Omega$$

For the PMOS device,

$$\begin{aligned} I_{Dsat} &= \frac{W_P \mu_{sat} C_{ox} (V_{DD} - |V_{TP}|)^2}{(V_{DD} - |V_{TP}|) + E_{CP} L_P} \\ &= \frac{(0.1)(10^{-4})8(10^6)1.6(10^{-6})(1.2 - 0.4)^2}{(1.2 - 0.4) + 2.4} \approx 25 \mu\text{A} \end{aligned}$$

$$\therefore R_{eqp} = \frac{1.2/2}{0.7(25 \mu\text{A})} = 33.5 \text{ k}\Omega$$

The HSPICE

Numbers of 12.5k-ohms

And 30k-ohm

Inverter – Resistance

- The value of T_{PHL} or T_{PLH} determine the value of the resistor (average on-resistance)
- Note that in the pull-down case (NMOS on) device starts in saturation (V_{DD} across its V_{DS} and might enter triode at some point, therefore it makes sense to define an effective resistance

$$R_{eqn} = 12.5 \text{ k}\Omega/\square$$

$$R_{eqp} = 30 \text{ k}\Omega/\square$$

$$R_N = R_{eqn} \times \frac{L_N}{W_N}$$


$$R_P = R_{eqp} \times \frac{L_P}{W_P}$$

Unit resistance of the devices (per square)


That is for a device with $L=W$ (obtained from HSPICE simulation), note the ration 2.4, does It remind of a number?

Total Resistance inversely proportional to W/L (remember that in triode region we could model the transistor simply with a resistor!

Inverter- Capacitances

 


One inverter driving another

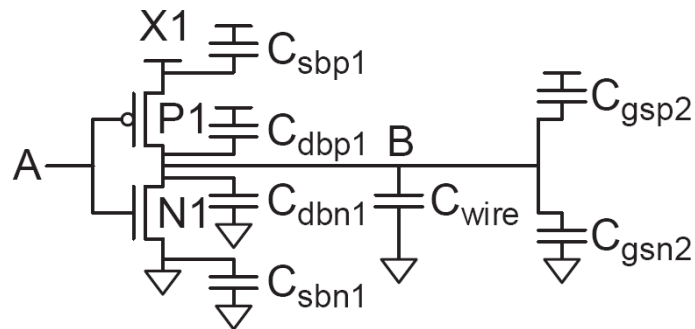

Showing all capacitances

 Capacitance relevant for delay calculation, i.e.
Sum of all capacitance at the output of first inverter





Equivalent Circuits for Transistors

- MOS transistor == Ideal switch + cap and ON resistance
- Unit nMOS has res R , cap C
- Unit pMOS has res $2R$, cap C
- Cap proportional to width
- Res inversely proportional to width
- Some capacitances may be shorted!

- Capacitance

  - $C = C_g = C_s = C_d = 2 \text{ fF}/\mu\text{m}$ of gate width in $0.6 \mu\text{m}$
- Gradually decline to $1 \text{ fF}/\mu\text{m}$ in 65 nm




FO1 Inv


*Assuming $C_{\text{eff}} = C_g = 1 \text{ fF/um}$ (if $C_g = 2 \text{ fF/um}$ we should keep them separate)

FO1 problem

 One inverter driving another
Identical inverter




(a)

 

(b)

Equivalent Circuit

 

(c)

Delay Calculation - Example


Delay Calculation for Inverter Driving Four Fanout Inverters

Problem:

A CMOS inverter has a pull-up device that is $8\lambda:2\lambda$ and a pull-down device that is $4\lambda:2\lambda$. It drives four identical inverters. Compute the inverter delay using $0.18\ \mu\text{m}$ technology parameters. Assume a ramp input and negligible wire capacitance.


Combinational MOS Logic

- Now that we understand the logic abstraction and the properties of valid logic gates, we can consider the issues of design basic building blocks of digital systems
- Typical combinational gate is a multiple input – single output system
- Performs Boolean operations on multiple input variables, drives one or more gates
- Design parameters and considerations:
 - Propagation delay
 - Static and dynamic power
 - Area
 - Noise margins (VTC)

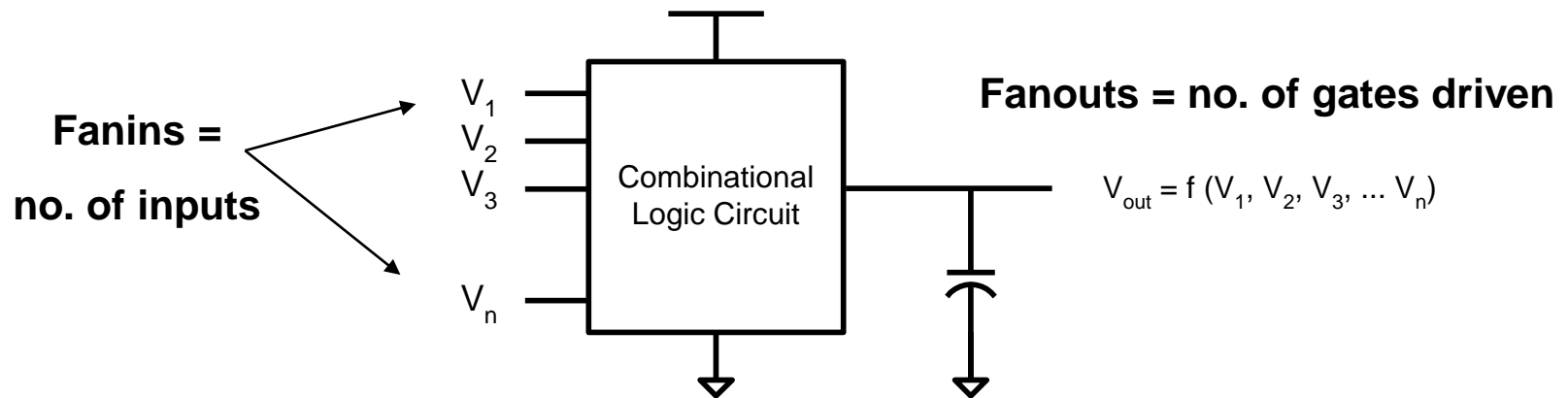


Pull-up and Pull-down Networks

 **Basic Structure
Of all CMOS logic gates**



- PMOS pull-up and NMOS pull-down networks are duals of each other
- Configuration of pull-up and pull-down networks create a current connection from the output to *either* V_{DD} or Gnd, based on the inputs
- PMOS devices have lower drive capability and thus require wider devices to achieve the same on-resistance as its pull-down counterpart

Static CMOS Logic Gates

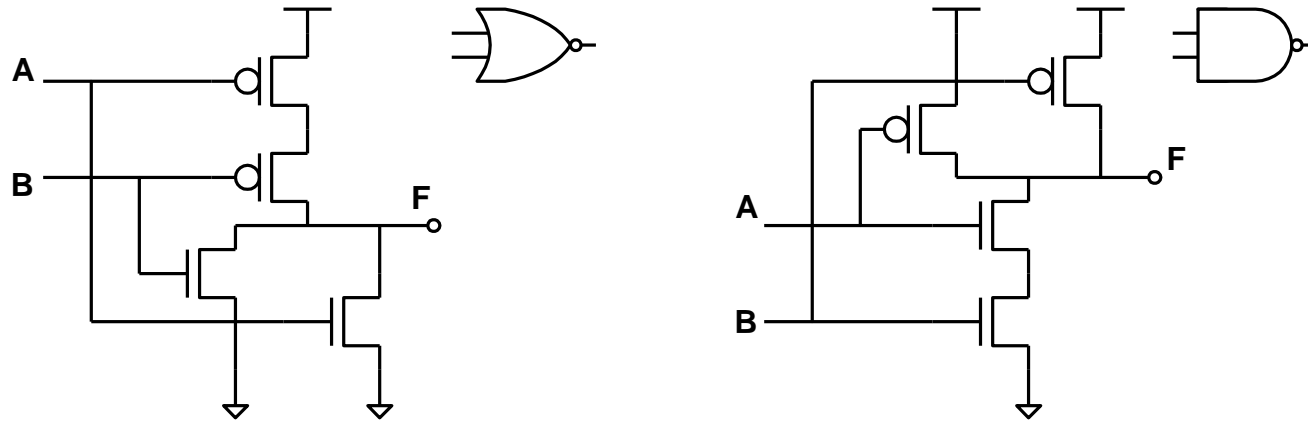


- These are the most common type of static gates
- Can implement any Boolean expression with these two gates
- Why is static CMOS so popular?
 - It's very robust!
 - it will eventually produce the right answer
 - Power, shrinking V_{DD} , more circuit noise, process variations, etc. limit use of other design styles

More Properties of Static CMOS Logic

- Fully complementary
- Low static power dissipation!
- Outputs swing full rail – V_{dd} (V_{OH}) to Gnd (V_{OL})
- Works fine at low V_{dd} voltages
 - But lower V_{dd} = less current = slower speed
- Combinational operation
 - Feed it some inputs, wait some delay, result comes out
 - No clocks required for normal operation
- Moderately good performance
 - Drive strength is proportional to transistor size
 - Large loads require large W
- Dual logic networks for N- and P-Channel devices


NAND and NOR Sizing

First Design Inverter

 


(a) Inverter

Then Map Results to Gates

 

(b) NAND

 


(c) NOR


- Drive strength determined by device widths - W (assume L is minimum size)
- For the moment, consider only C_L (we are ignoring the device self-capacitance)
 - Pick the right sizes for the basic inverter and then assign values to gates
 - What does that mean for parallel and series combinations?
 - For parallel transistors, direct mapping from inverter
 - For series transistors, need to compute equivalent sizes

Equivalent Sizes - NAND


 
Consider a three-input NAND gate (NMOS portion only):




VTC and Noise Margins – NAND and NOR

 


NOR gate

  

NAND gate

 

Load Capacitance for NAND and NOR

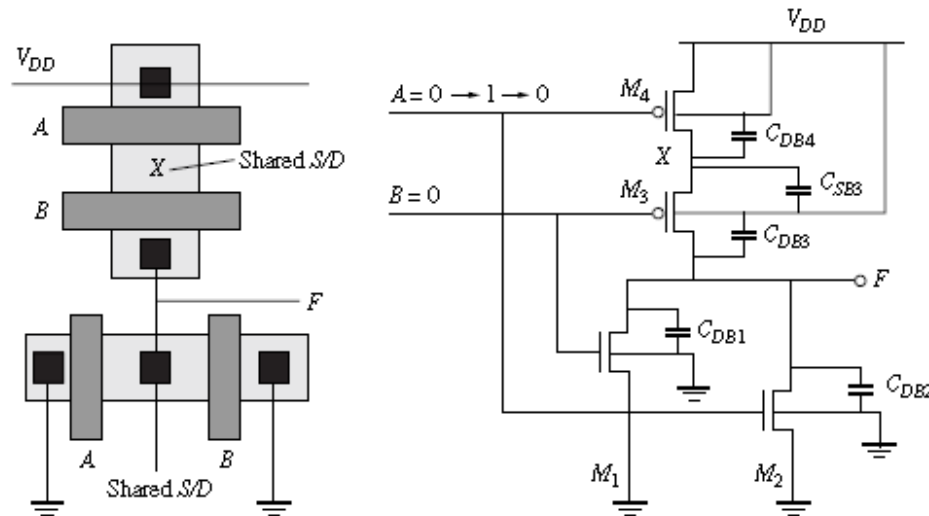

What is worst-case capacitance calculations, why does it matter for speed calculations?

$$\begin{aligned}
 C_{\text{self}} &= \underbrace{C_{DB1} + C_{DB2}}_{n^+ \text{ shared S/D}} + C_{DB3} + \underbrace{C_{SB3} + C_{DB4}}_{p^+ \text{ shared S/D}} \\
 &= C_{DB12} + C_{DB3} + C_{SDB34}
 \end{aligned}$$

Example: what is the worst case input and output capacitance for a NAND3 CMOS gate
(Board Notes)

Complex Logic Circuits

- The ability to easily build complex logic gates is one of the most attractive features of MOS logic circuits
- Design principle of the pull-down network:
 - OR operations are performed by parallel connected drivers
 - AND operations are performed by series connected drivers
 - Inversion is provided by the nature of MOS circuit operation
- Don't get too carried away... Use this knowledge wisely
 - Remember that complex functions don't have to be implemented with a single gate
 - Can break up very complicated Boolean expressions into a cascade of gate stages
 - Limit series stacks to 3~4
- We will use De Morgan's Law to build the dual networks

Review of DeMorgan's Law

$$\begin{array}{c} \text{a} \\ \text{b} \end{array} \text{ AND } = \begin{array}{c} \text{a} \\ \text{b} \end{array} \text{ OR } \quad \overline{ab} = \overline{a} + \overline{b}$$

$$\begin{array}{c} \text{a} \\ \text{b} \end{array} \text{ OR } = \begin{array}{c} \text{a} \\ \text{b} \end{array} \text{ AND } \quad \overline{a} \overline{b} = \overline{a + b}$$

- De Morgan's theorem:

The complement of any logic function is found by complementing all input variables and replacing all AND operations with OR and all OR operations with AND

Circuit Design Rule

- Use De Morgan's law to find the complement of a function for the pull-down network
- Use Duality to find the pull-up network

Complex CMOS Gate Design Example


- Implement an AND-OR-INVERT (AOI) function

$$Z = \overline{A \cdot B + C}$$


- Get the expression into forms that enable easy implementation of pull-up and pull-down networks

$$\overline{Z} = (A \cdot B + C)$$


 
$$Z = (\overline{A} + \overline{B}) \cdot \overline{C}$$



Complement of Z

 


Dual of Complement of Z

  


Combine Results

XOR and XNOR Gates

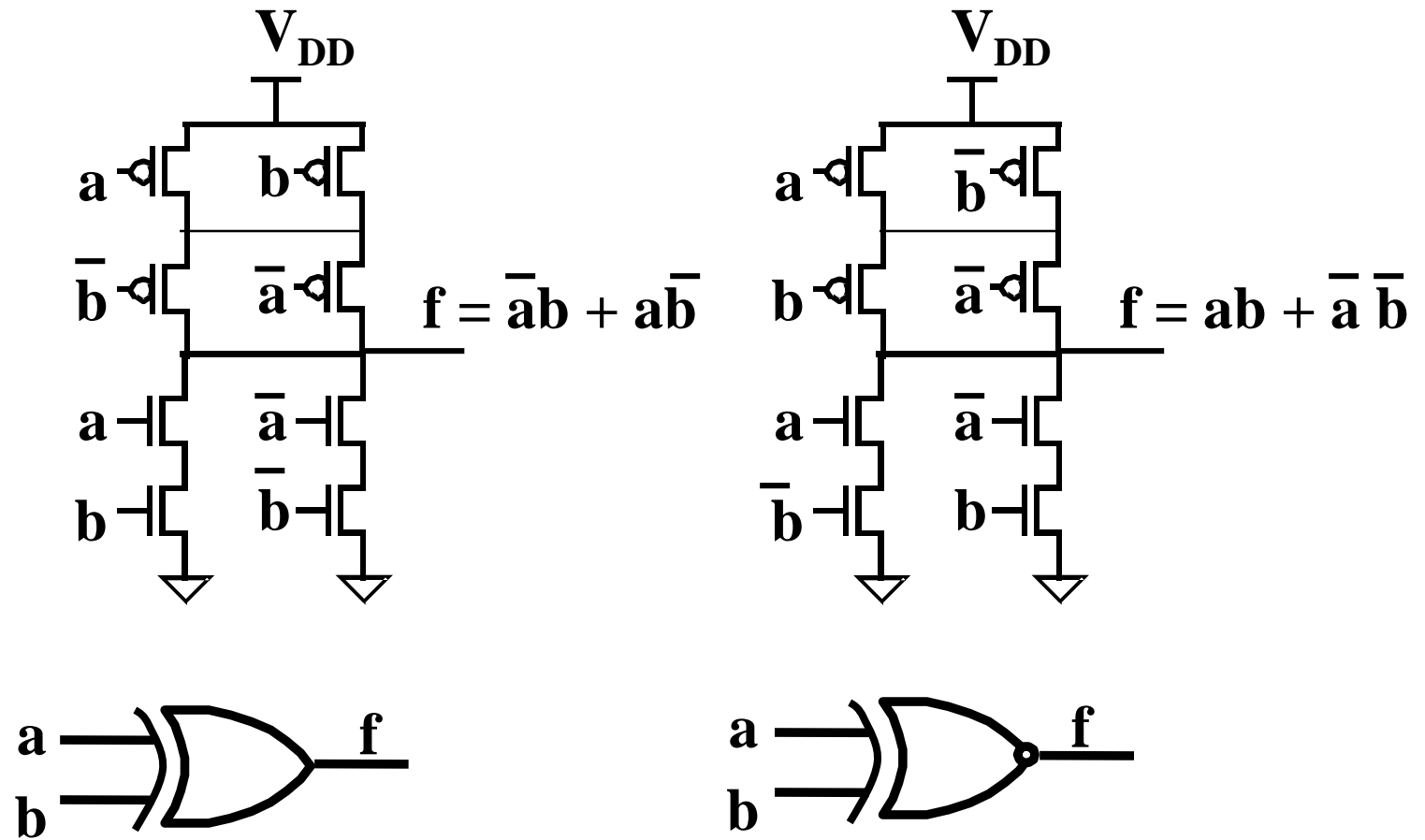


CMOS Multiplexer

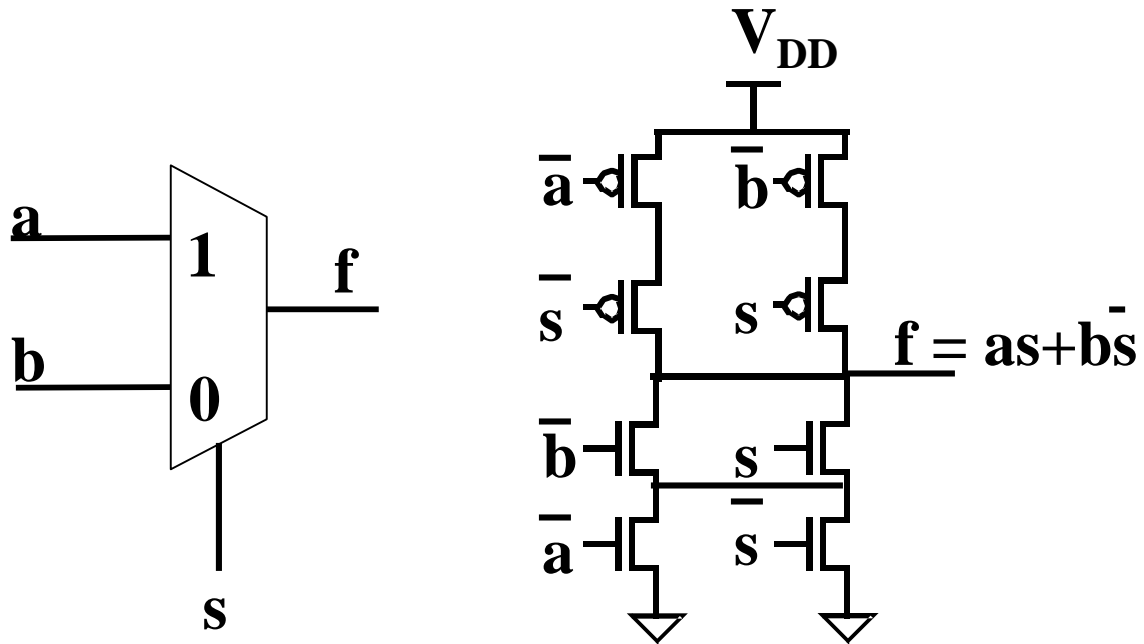


The Bad News

- Slows down dramatically for large fanins due to long series stack of transistors
 - fanin = number of inputs
 - PMOS series stacks worse than nMOS series stacks
- Large number of transistors
 - $2n$ devices for n -input NAND
 - At least 2 devices per input
- Bigger layout
 - $n+$ to $p+$ spacing rule and well spacing rule
 - Large device sizes required to counteract series stack
- Limit the fanin to 3 or 4...or delay and area will be too large


Eight-Input AND gate

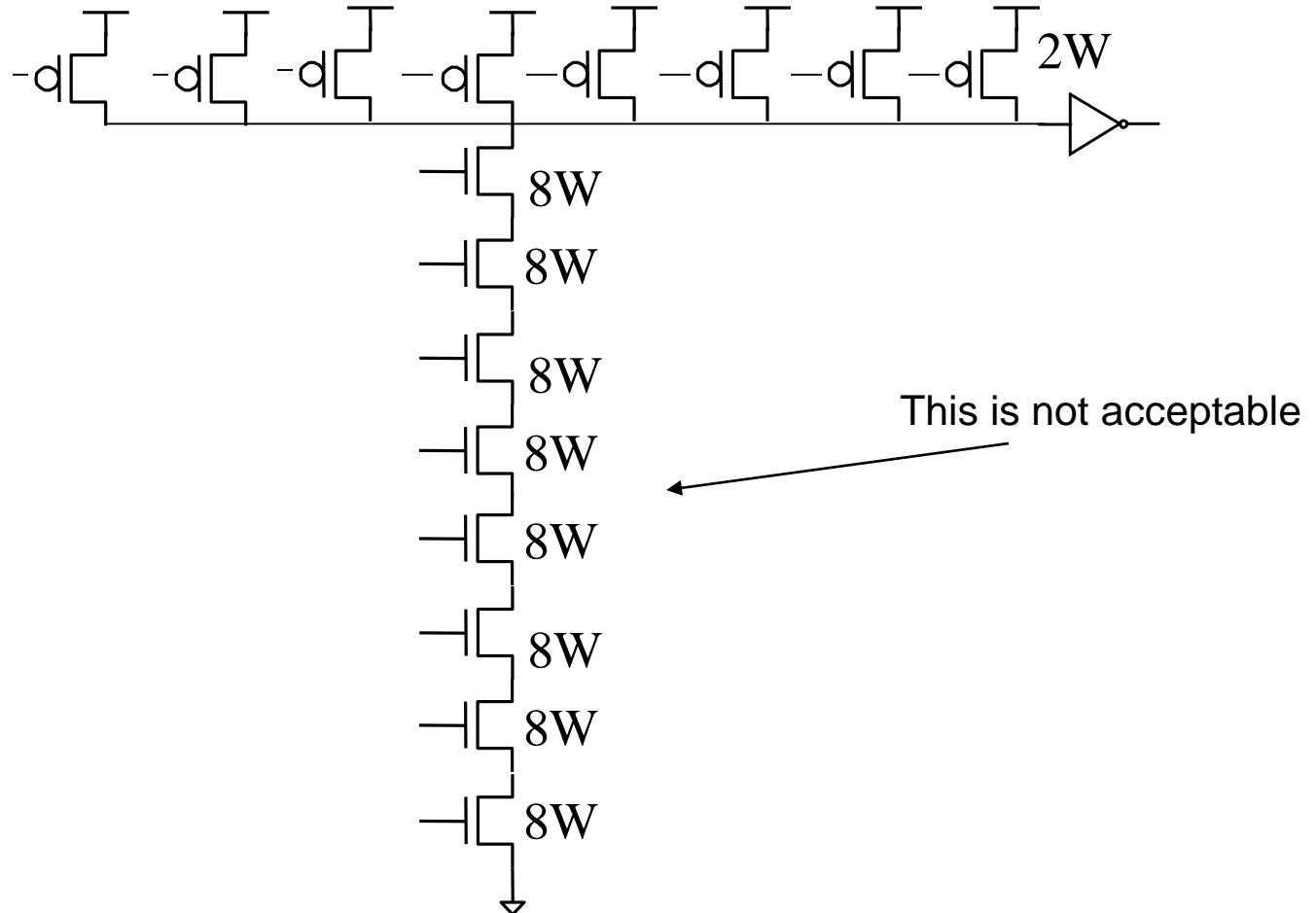

Multi-level Logic Implementations

 



NAND2-INV-NAND2-INV

 

NAND2-NOR2-NAND2-INV

- There are many more options to try
- Better than stacked version but signal has to travel through multiple stages



Pseudo-NMOS Logic – NOR gate

  

A	B	Z
0	0	1
0	1	0
1	0	0
1	1	0

- Design issues:
 - Sizing Ratio
 - Ratio pull-up to pull-down (V_{OL} & V_{OH})
 - Propagation delay
 - Subthreshold current can degrade V_{OH} slightly
 - V_{OL} decreases as more devices turning on

Pseudo-nMOS Logic – NAND Gate

  


A	B	Z
0	0	1
0	1	1
1	0	1
1	1	0




- Issues
 - Sizing Ratio
 - Need to make pull-down devices wider
 - Parasitic cap goes up with bigger devices
 - Lower devices in stack slower compared to upper ones because they see more capacitance

Back to AND8 Option - Use Pseudo-NMOS

Inputs are
Inverted, not
shown here

 

Bubble pushing

   

No need for long stack of devices

Properties of Static Pseudo-NMOS Gates

- DC power
 - always conducting current when output is low
- V_{OL} and V_{OH} depend on sizing ratio and input states
- **Poor low-to-high transition**
- Large fanin NAND gates tend to get big due to ratioing
- As transistor count increases, power consumption is too high
 - Cannot use this approach for all gates on the chip
- But what are its advantages?
 - Good for wide NOR structures
 - Memory decoder
 - Smaller number of transistors (area) / logic function